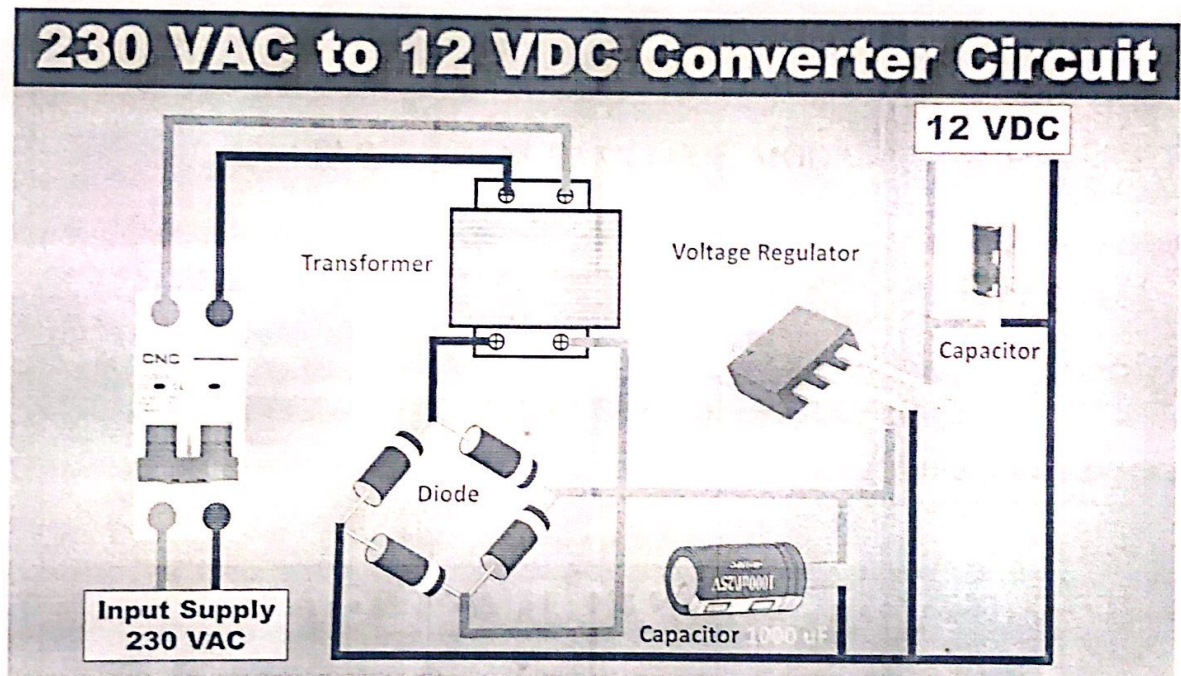


230V AC to 12V DC POWER SUPPLY CIRCUIT

SUBMISSION PRESENTED TO
SIR P.T. SCIENCE COLLEGE, MODASA

Project Report

PHYSICS Sem II



SIR P.T. SCIENCE COLLEGE, MODASA-383 315

APRIL - 2023





Project Report

Submitted to,
Department of Physics

Supervisor

Dr. G. L. Vekaria (M.Sc. M. Phil. Ph.D.)



SIR P. T. SCIENCE COLLEGE

MODASA – 383315


April – 2023

SIR P.T.SCIENCE COLLEGE, MODASA

(Managed by THE M. L. GANDHI HIGHER EDUCATION SOCIETY)

[UGC 2F, 12B RECOGNISED]- [NAAC- ACREDITED B⁺⁺]

CERTIFICATE

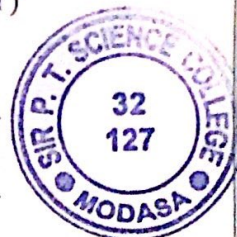


This is to certify that the project work entitled '**230V AC to 12V DC POWER SUPPLY CIRCUIT**' is carried out by students mentioned below. The Project work allotted them first year Bachelor of Science during the academic year 2022-2023. The project has been approved as it satisfies the academic requirements in respect of project work prescribed for the first year Bachelor of Science

SR NO.	NAME	RollNo.
1	Aksheshkumar Dilipkumar Prajapati	1001
2	Amita Dineshbhai Chaudhari	1002
3	Ankitkumar Navinbhai Damor	1003
4	Ankitkumar Vinodbhai Bhoi	1004
5	Ayushiben Sureshbhai Od	1005
6	Bhargavkumar Hiteshbhai Patel	1006
7	Dhruv Mukeshbhai Patel	1007
8	Dhruviben Lalsinh Rahevar	1008
9	Hiteshkumar Mukeshbhai Patel	1009
10	Kathankumar Sandipbhai Upadhyay	1010
11	Krunal Chimanbhai Patil	1011
12	Krupaben Jiteshchandra Pandya	1012
13	Mahetabbanu Hamidbhai Ghanchi	1013
14	Meera Asvinbhai Patel	1014
15	Piyushbhai Laxmanbhai Panchal	1015
16	Rayhan Mohammedhanif Malek	1016
17	Rinkaben Babubhai Damor	1017
18	Ronak Sunilkumar Chaudhary	1018
19	Rutviben Dharmendrabhai Sagar	1019
20	Sahilkumar Bharatbhai Patel	1020
21	Sumit Jivabhai Bhagora	1021
22	Sumitraba Arvindsinh Jadeja	1022

23	Tanvee Tarunkumar Kadia	1023
24	Umeshkumar Kantibhai Pandor	1024
25	Vivekkumar Dharmendrabhai Pagi	1025
26	Vivekkumar Rasikbhai Khant	1026
27	Yashpalsinh Chhatrasinh Rathod	1027
28	Aamena AbdulRehman Bayadiya	1201
29	Aamena Zakirhusen Patel	1202
30	Abhaykumar Surpalbhai Kotwal	1203
31	Aesha Yogeshkumar Bhatiya	1204
32	Ajaykumar Dhirubhai Bamaniya	1205
33	Akshaykumar Bharatbhai Dabhi	1206
34	Alpeshbhai Babubhai Pagi	1207
35	Amiben Bipinchandra Mesriya	1208
36	Amishaben Natvarsinh Makvana	1209
37	Anjaliben Amratbhai Pranami	1210
38	Archana Mukeshbhai Patel	1211
39	Archi Pinalkumar Sevak	1212
40	Archnababen Rajubhai Damor	1213
41	Arman Chandubhai Yogi	1214
42	Arti Dhulabhai Patel	1215
43	Arvindbhai Kantibhai Damor	1216
44	Aryan Kanubhai Parmar	1217
45	Ashwinkumar Laxmanbhai Machhar	1218
46	Avaniben Nandubhai Damor	1219
47	Avinashkumar Ashokbhai Kharadi	1220
48	Bhartibahen Rajubhai Damor	1221
49	Bhavanaben Pravinbhai Damor	1222
50	Biren Vipulkumar Damor	1223
51	Brijeshkumar Chimanbhai Bariya	1224
52	Chinkalben Kantibhai Sutariya	1225
53	Chiragkumar Nileshbhai Kharadi	1226
54	Devkumar Maheshbhai Patel	1227
55	Dhanrajsinh Upenrasinh Chauhan	1228
56	Dharalbahen Popatbhai Pandor	1229
57	Dharatiben Ramanbhai Damor	1230
58	Dhrumi Kiritbhai Valand	1231




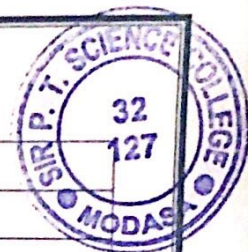

59	Digvijaysinh Narendrasinh Rathod	1232
60	Dimpalbaben Chandubhai Raval	1233
61	Dipakbhai Vikrambhai Bariya	1234
62	Dishaben Bhupatsinh Zala	1235
63	Diya Sanjaykumar Patel	1237
64	Fatema Mohammedhabib Jethra	1239
65	Fizarparveen Mohammedaslam Kazi	1240
66	Haniben Hasmukhbhai Patel	1241
67	Hardikkumar Parvatbhai Machhar	1242
68	Harmil Mukeshbhai Prajapati	1243
69	Harshilkumar Nareshbhai Pranami	1244
70	Harshkumar Dilipbhai Parmar	1245
71	Harvi Subhashchandra Patel	1246
72	Hasmukhkumar Shankarbhai Patel	1247
73	Hemangkumar Kalpeshbhai Prajapati	1248
74	Het Hiteshkumar Patel	1249
75	Hetalben Kamleshbhai Damor	1250
76	Hetvi Nareshkumar Patel	1251
77	Himani Jagdishbhai Panchal	1252
78	Hirenkumar Lalitbhai Katara	1254
79	Hiteshkumar Jesingbhai Damor	1255
80	Jaiviben Ghanshyambhai Patel	1256
81	Janak Jaydevbhai Prajapati	1257
82	Janaviben Karansinh Dabhi	1258
83	Jankiben Maeshbhai Panchal	1259
84	Janvi Kamleshbhai Chaudhari	1260
85	Jay Mohanbhai Bhagora	1261
86	Jigarbhai Kantibhai Suvera	1262
87	Jyotikaben Surpalbhai Khokhariya	1263
88	Kalprajsinh Dilipsinh Sisodiya	1264
89	Kamleshkumar Pujabhai Katara	1265
90	Karanbhai Jashvantbhai Parmar	1266
91	Kartavyakumar Jashvantbhai Darji	1267
92	Kashish Rohitkumar Bhoi	1268
93	Kashyapkumar Mukeshbhai Patel	1269
94	Kevalkumar Pareshbhai Patel	1270



95	Keyur Mahendrabhai Gohel	1271
96	Keyurkumar Dineshbhai Taral	1272
97	Khalidabanu Javidhusen Piprani	1273
98	Khushbu Jasvantlal Chaudhari	1274
99	Khushbuben Shaileshkumar Manat	1275
100	Khushi Rameshbhai Parmar	1276
101	Khushibahen Navnitbhai Vankar	1277
102	Krish Girishbhai Pandya	1279
103	Krish Rateshbhai Patel	1280
104	Krish Arvindkumar Patel	1281
105	Krish Ashvinbhai Rathod	1282
106	Krish Sanjaykumar Patel	1283
107	Krishna Jayeshkumar Kavathia	1285
108	Krunal Parshottambhai Vaghela	1286
109	Krupaben Shankarbhai Manat	1287
110	Mahammadaamir Jakirhusen Zaz	1289
111	Maitreykumar Bipinchandra Bharvad	1290
112	Manasveeben Kaushikkumar Patel	1291
113	Manojbhai Ashvinbhai Ninama	1292
114	Mansiben Kanubhai Prajapati	1293
115	Mittal Bharatsinh Zala	1294
116	MohammadFahim Junedbhai Bavan	1295
117	MohammadFaiyaz Mahammedsharif Baloch	1296
118	Mohammed rizwan Mohammedrafik Chauhan	1297
119	Muhammad Hamza Nasirhusen Chauhan	1298
120	Namra Vinodkumar Patel	1299
121	Naznin Gulammahammed Patel	1300
122	Nehaben Rameshbhai Tarar	1301
123	Nilamben Vikramsinh Solanki	1302
124	Nureaqsha MoSajid Saiyed	1303
125	Palakben Dilipbhai Raval	1304
126	Palakben Vijyasinh Hada	1305
127	Palakkumari Prabhudas Patel	1306
128	Parth Narsinhbhai Gameti	1307
129	Parthiv Yogeshbhai Pandya	1308
130	Parulben Bhathibhai Damor	1309

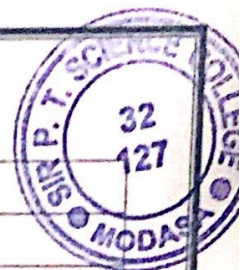

131	Parvatbhai Haribhai Damor	1310
132	Pinkeshkumar Natvarbhai Darji	1311
133	Pooja Hemantkumar Patel	1312
134	Prachiben Bharatbhai Damor	1313
135	Pradipbhai Babubhai Chauhan	1314
136	Pragnesh Bharatbhai Prajapati	1315
137	Pragnesh Dahyabhai Prajapati	1316
138	Prinsi Atishbhai Patel	1317
139	Priyabahen Maheshbhai Panchal	1318
140	Priyankaben Amrabhai Damor	1319
141	Priyanshiben Rajeshkumar Khokhar	1320
142	Purva Dineshbhai Prajapati	1321
143	Radhabahen Udabhai Bariya	1322
144	Radhaben Rameshbhai Damor	1323
145	Raginiben Bharatbhai Prajapati	1324
146	Rajavee Mitulkumar Patel	1325
147	Rajvi Kanubhai Parmar	1326
148	Ranjitbhai Kalubhai Damor	1327
149	Ranjitsinh Rameshbhai Damor	1328
150	Ravikumar Dilipbhai Vanajara	1329
151	Rekhaben Bharatbhai Katara	1330
152	Rim Prabhudas Chaudhari	1331
153	Riya Ketankumar Patel	1332
154	Sahil Premjibhai Parmar	1333
155	Samarth Anantkumar Yadav	1334
156	Saniya Mfarid Mistri	1335
157	Saumya Dharmendrabhai Chaudhary	1336
158	Shafiyah Mohammadhanif Baloch	1337
159	Shailee Arvidnbhai Chaudhari	1338
160	Shanikumar Sanjaybhai Prajapati	1339
161	Shifaben MohammadHabib Chadi	1340
162	Shyamliben Bhembhai Khant	1341
163	Siddhiben Dilipkumar Nayak	1342
164	Simaben Sukhabhai Khant	1343
165	Smit Jitendrabhai Patel	1344
166	Smit Maheshkumar Prajapati	1345

167	Somiben Valabhai Damor	1346
168	Suhaskumar Manabhai Dama	1347
169	Tanvikunvarba Vinaysinh Puwar	1349
170	Tirthkumar Mahendrabhai Patel	1350
171	Trisha Shailendrasinh Zala	1351
172	Truptiben Mukeshbhai Sutariya	1352
173	Vaibhavkumar Rameshbhai Parmar	1353
174	Vaideheeben Hareshkumar Prajapati	1354
175	Vanraj Kumar Somabhai Damor	1355
176	Vanshika Sanjaykumar Bhoi	1356
177	Vashishthbhai Kamleshbhai Patel	1357
178	Vedantkumar Jayantibhai Prajapati	1358
179	Vidhyabahen Virendrabhai Patel	1359
180	Vinaybhai Valambhai Gameti	1360
181	Vishalbhai Rameshbhai Raval	1361
182	Vraj Kamleshkumar Jayswal	1362
183	Vrushiben Baratbhai Suthar	1363
184	Yatri Narendrabhai Patel	1364
185	Yuvrajsinh Dharmendrasinh Parmar	1365

PLACE: MODASA

SIGNATURE OF GUIDE

G. L. Vekaria
 PROF. G. L. VEKARIA

SIGNATURE OF H.O.D.

DR. R. H. Parmar
 DR. R. H. PARMAR



Sir P. T. Science College
 Modasa-383315, Dist. Arvali.

ACKNOWLEDGEMENT

This project work has been inspiring often exciting, sometimes challenging but always interesting And an enjoyable experience.

The success comes from experience and experience comes from bad experience and great failure. But bad experience is like carbon, in every polish it will give the shine and be a "diamond". Now we remembering with gratitude those hands behind the success of our project which really pushed us to cross the failure and inspiring to us.

First thank to our H.O.D .Dr. R.H.PARMAR for giving us such a genius guide and inspiration. We thank to our genius guide PROF. G. L. VEKARIA for supporting us in every difficulty. He gives us the deeply guidance according to present project work.

We also thankful to our Sir P.T. Science College, Physics Department, for providing necessary components at any stage without any hesitation.

All these thanks are, however, only a fraction of what is due to almighty for granting us an opportunity and strength to successfully accomplish this assignment.

OBJECTIVE

1. To design the circuit for variable dc power supply that varies 2v to 15 v & 2A current using IC LM317. 2. To observe the output to meet the requirement.

MATERIAL REQUIRED

[A] Components


1. Transformer 240v 50 HZ (6v-0.5mA)
2. 4 diode 1N4007
3. 10 μ F/50v capacitor
4. 0.01 μ F(103)capacitor
5. LM317T IC
6. Variable resistor 1k Ω & 10k Ω
7. 1K Ω /1W resistor

[B] Apparatus


1. Power supply
2. Multimeter
3. PCB
4. Connection wires
5. Wire cuter
6. Soldering Iron

CIRCUIT DIAGRAM



5V DC Power Supply Circuit using LM317

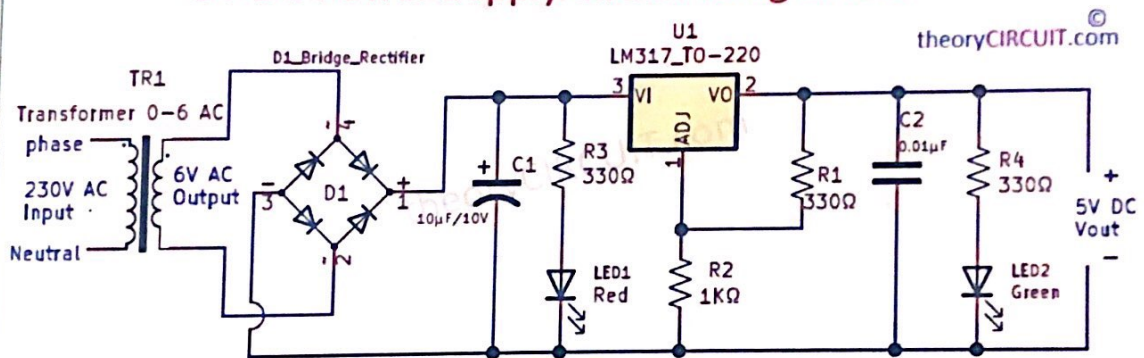


THEORY & WORKING

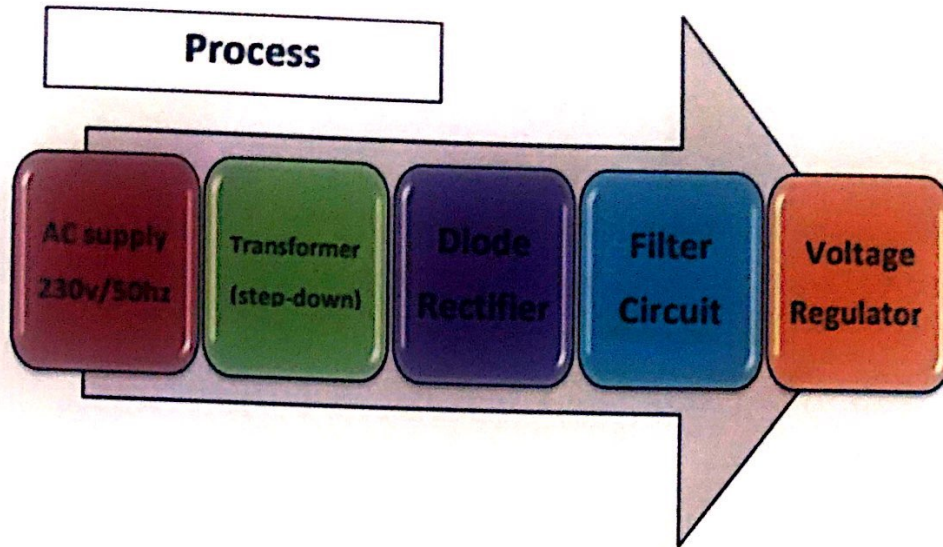


Transformer: -

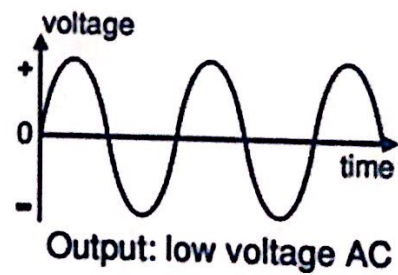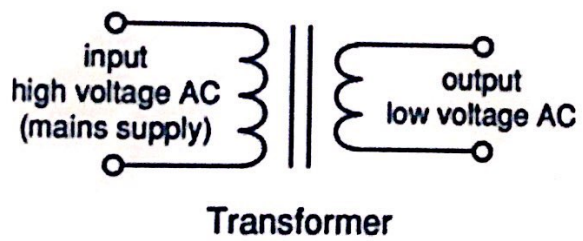


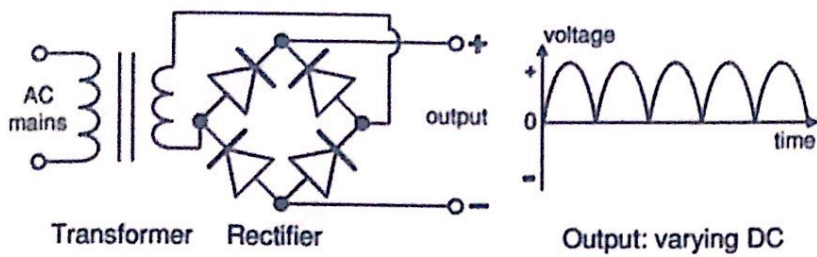

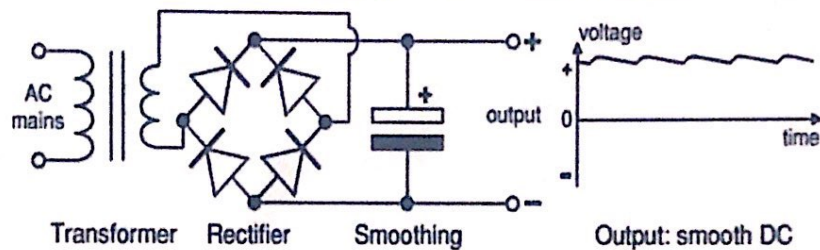Transformer + Rectifier + Smoothing: - The smooth DC output has a small ripple.



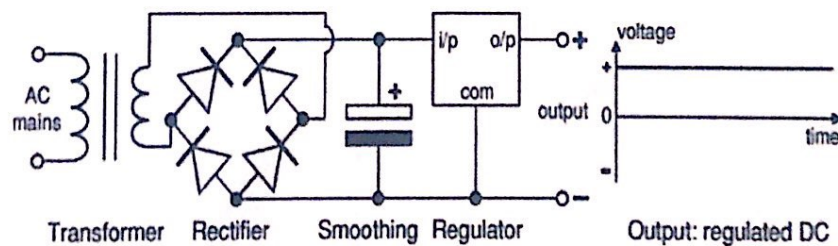Transformer + Rectifier + Smoothing + Regulator: - The regulated DC output is very smooth with no ripple. It is suitable for all electronic circuits.



Transformer

A Transformer is an equipment used either for raising or lowering the voltage of an ac supply with a corresponding decrease and increase in current. It essentially consist of two windings primary and secondary

N_1 : no. of turns in primary coil

N_2 : no. of turns in secondary coil

$N_1 < N_2$:- Step-up transformer

$N_1 > N_2$:- Step-down transformer Transformers convert

AC electricity from one voltage to another with little loss of power. Transformers work only with AC and this is one of the reasons why mains electricity is AC.

Step-up transformers increase voltage, step-down transformers reduce voltage. Most power supplies use a step-down transformer to reduce the dangerously high mains voltage (230v) to safer low voltage.

The input coil is called the primary and the output coil is called the secondary. There is no electrical connection between the two coils, instead they are linked by an alternating magnetic field created in the soft-iron core of the transformer. The two lines in the middle of the circuit symbol represent the core. Transformers waste very little power so the power out is (almost) equal to the power in. Note that as voltage is stepped down current is stepped up. The ratio of the number of turns on each coil, called the turn's ratio, determines the ratio of the voltages. A step-down transformer has a large number of turns on its primary (input) coil which is connected to the high voltage mains supply, and a small number of turns on its secondary (output) coil to give a low output voltage.


Rectifier

There are several ways of connecting diodes to make a rectifier to convert AC to DC. The bridge rectifier is the most important and it produces full-wave varying DC. A full-wave rectifier can also be made from just two diodes if a centre-tap transformer is used, but this method is rarely used now that diodes are cheaper. A single diode can be used as a rectifier but it only uses the positive (+) parts of the AC wave to produce half-wave varying DC.

Bridge Rectifier

A bridge rectifier can be made using four individual diodes, but it is also available in special packages containing the four diodes required. It is called a full-wave rectifier because it uses all the AC wave (both positive and negative sections).

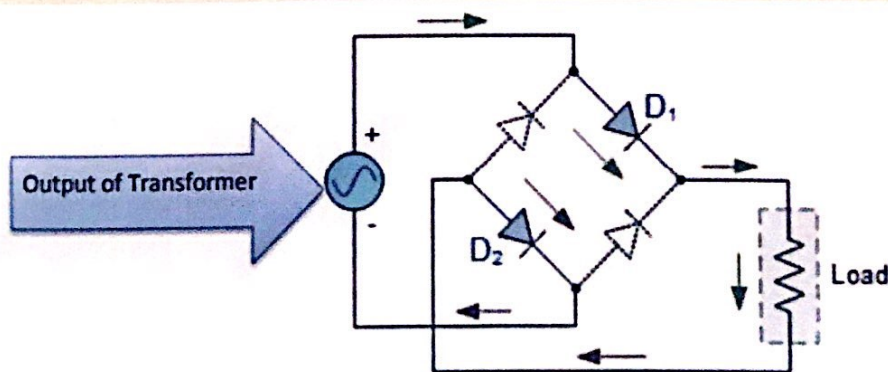Working of Full Wave Bridge Rectifier:- The Positive Half-cycle. During the positive half cycle of the supply, diodes D1 and D2 conduct in series while diodes D3 and D4 are reverse biased and the current flows through the load as shown below



The Negative Half-cycle During the negative half cycle of the supply, diodes D3 and D4 conduct in series, but diodes D1 and D2 switch "OFF" as they are now reverse biased. The current flowing through the load is the same direction as before.


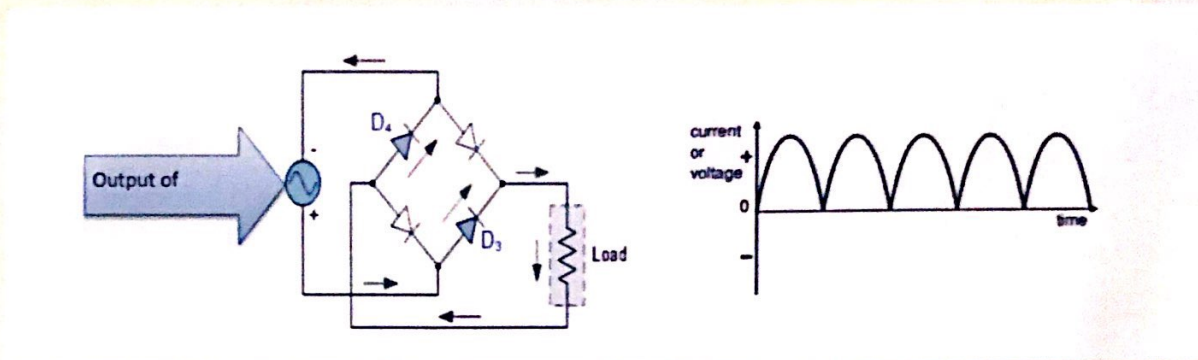


Fig: Resultant wave form

Hence, we can say that the bridge wave rectifier give the pulsating DC voltage which are not suitable for electronics circuit.


Smoothing (Filter):-

Smoothing is performed by a large value electrolytic capacitor connected across the DC supply to act as a reservoir, supplying current to the output when the varying DC voltage from the rectifier is falling. The diagram shows the unsmoothed varying DC (dotted line) and the smoothed DC (solid line). The capacitor charges quickly near the peak of the varying DC, and then discharges as it supplies current to the output.

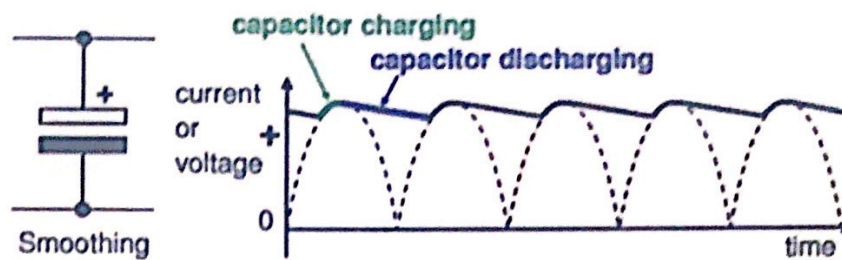

Note:- Note that smoothing significantly increases the average DC voltage to almost the peak value ($1.4 \times \text{RMS value}$). Smoothing is not perfect due to the capacitor voltage falling a little as it discharges, giving a small ripple voltage. For many circuits a ripple which is 10% of the supply voltage is satisfactory and the equation below gives the required value for the smoothing capacitor. A larger capacitor will give less ripple. The capacitor value must be doubled when smoothing half-wave DC. So, in this we concluded that the pulsating DC voltage is applied to the smoothing capacitor. This smoothing capacitor reduces the pulsations in the rectifier DC output voltage. The smooth DC output has a small ripple. It is suitable for most electronics circuits.

Voltage Regulation:(using IC LM317) Output from the full wave bridge rectifier is fed to a LM317 regulator IC. LM317 provides varied voltage from 1.2V to 35V. Reference voltage of 1.25 V is maintained at 220 ohm Resistor. The LM317 Voltage Regulator is a 3-terminal adjustable voltage regulator which can supply an output voltage adjustable from 1.2V to 35V. It can supply more than 1.5A of load current to a load. LM317 Pinout The LM317 Voltage Regulator has 3 pins. Below is the pinout:

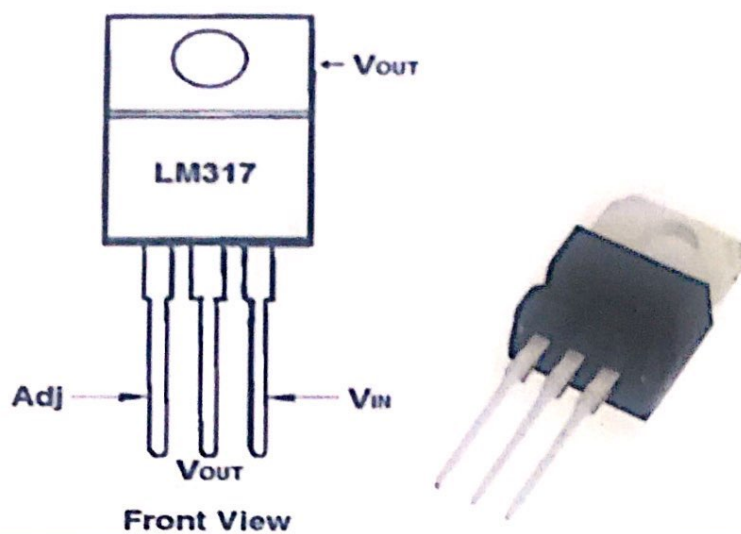

Looking from the front of the voltage regulator, the first pin (on the left) is the Adjustable Pin, the middle is V_{OUT} , and the last pin (on the right) is V_{IN} . V_{IN} - V_{IN} is the pin which receives the incoming voltage which is to be regulated down to a specified voltage. For example, the input voltage pin can be fed 12V, which the regulator will regulate down to 10V. The input pin receives the incoming, unregulated voltage. Adjustable - The Adjustable pin (Adj) is the pin which allows for adjustable voltage output. To adjust output, we swap out resistor R_2 value for a different resistance. This creates adjustable voltages. V_{OUT} - V_{OUT} is the pin which outputs the regulated voltage. For example, the LM317 may receive 12V as the input and output a constant 10V as output.

CAPACITORS C2 & C3 :-

The capacitors C2 (0.1 uF) and C3(10 uF) are used to clean up the power line. C2 is optional and it's used to clean up transient response. C3 is needed if the device is far from any filter capacitors. This capacitors help smooth out the power supply line in case of abrupt current spikes. C2-0.1uF (Ceramic Capacitor or Mylar Capacitor) reduces noise.

The C4 - 470uF 25V (electrolytic capacitors) acts like a miniature battery that supplies power during the spike

$$V_{out} = V_{ref} + \left(1 + \frac{R_L}{R_n}\right)$$

$$V_{ref} = 1.25V$$

$$R_L = 1K\Omega$$

$$R_n = 330\Omega$$


$$V_{out} \approx 5V$$

FABRICATION PROCESS


Electrical Fabricating, consisting of electrical design i.e. making PCB, soldering, is making connection correctly etc. Various Tools & Equipment Needed For Fabrication



Soldering wire

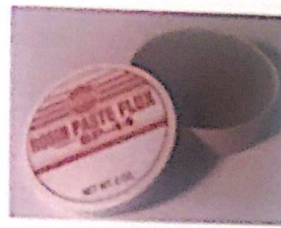

flux

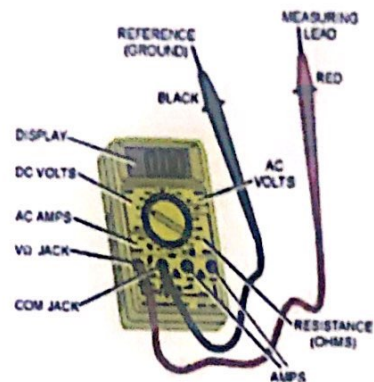

Soldering

Soldering is a process in which two or more metal items are joined together by melting and flowing a filler metal into the joint, the filler metal having a relative low melting point. Soft soldering is characterized by the melting point of the filler metal, which is below 4000 C (7520F). The filler metal used in the process is called solder. In a soldering process, heat is applied to the parts to be joint by capillary action and to bond to the materials to be joined by wetting action. After the metal cools, the resulting joints are not as strong as the base metal, but have adequate strength.

Tips & Tricks Soldering is something that needs to be practiced. These tips should help you begin successful so you can stop practicing and get down to some serious building. 1. Keep the iron tip clean. A clean iron tip means better heat conduction and a better joint. Use a wet sponge to clean the tip between joints. 2. Double check points. It is good idea to check all the solder joints with an Ohm meter after they are cooled. If the joint measures any more than a few tenths of an ohm, then it may be a good idea to resolder it. 3. Use the proper iron. Remember that bigger joints will take longer to heat up with an 30W iron than with a 150w Iron. 4. Solder small parts first. Solder resistors , jumper leads, diodes and any other small parts before you solder larger parts like capacitors and transistors. This makes assembly much easier.

A constant current source in electronics is a device/circuit that produces a constant value of current regardless of source voltage or load resistance. Here we design a simple and easy constant current DC power supply circuit using Three terminal adjustable regulator IC LM317. This circuit will provide different voltage output according to the input voltage and constant current output depends on the value of reference resistor R1.

Hardware Components

The following components are required to make DC Power Supply Circuit

S. No	Components	Value	Qty
1	Transformer	0-9V DC Output	1
2	Regulator IC	LM317	1
3	Diode	1N4007	4
4	Electrolytic Capacitor	100 μ F/16V	1
5	Ceramic Capacitor	0.1 μ F	1
6	Resistor (Depend on Load)		1

Working Explanation

As we can see in the circuit, first we need to build a rectifier circuit by implementing a step-down transformer and bridge rectifier to make a constant current DC power supply. Here we used 230V input primary, 0-9V AC secondary step-down transformer, and 1N4007 diode to form a bridge rectifier. Capacitors C1 and C2 are placed as a filter to remove AC ripples from the DC supply, then to regulate the current output we used an IC LM317.

IC LM317 from Texas Instruments is a three-terminal adjustable regulator and it can handle output current up to 1.5A it has internal short circuit current limiting options and a thermal overload protection circuit. Now the adjusted terminal of LM317 is connected with the output load after the R1 reference resistor and it functions as current feedback. In the prototype circuit, we used a 10Ω / 5W resistor and obtained a 125mA constant current output DC power supply.

$$I_{out} = V_{ref}/R1$$

$V_{ref} = 1.25V$ for LM317 we can calculate the R1 resistor value with this formula, the R1 resistor value depends on your current output requirements.

Applications

These are useful for laser and electroplating applications.

A regulated Power supply (RPS) is an embedded circuit, used to convert unregulated alternating current into a stable direct current by using a rectifier. The main function of this is to supply a constant voltage to a circuit that should be functioned in a particular power supply limit.

Mobile phone chargers.

Regulated power supplies in different application.

Various oscillators and amplifiers